

# Hands-on Lab 3: Motion

EECS 16B Fall 2022

Slides: [links.eecs16b.org/lab3-slides](https://links.eecs16b.org/lab3-slides)

# Administrivia


- Be a good team member, make sure you are contributing to the group

# Lab 3 Overview


- Build and test motor controller circuits
  - Pulse Width Modulation (PWM) from Arduino
  - Bipolar Junction Transistor (BJT)
  - Switch
  - Diode
- Install and test encoders
  - Sensing the distance traveled and speed of the car
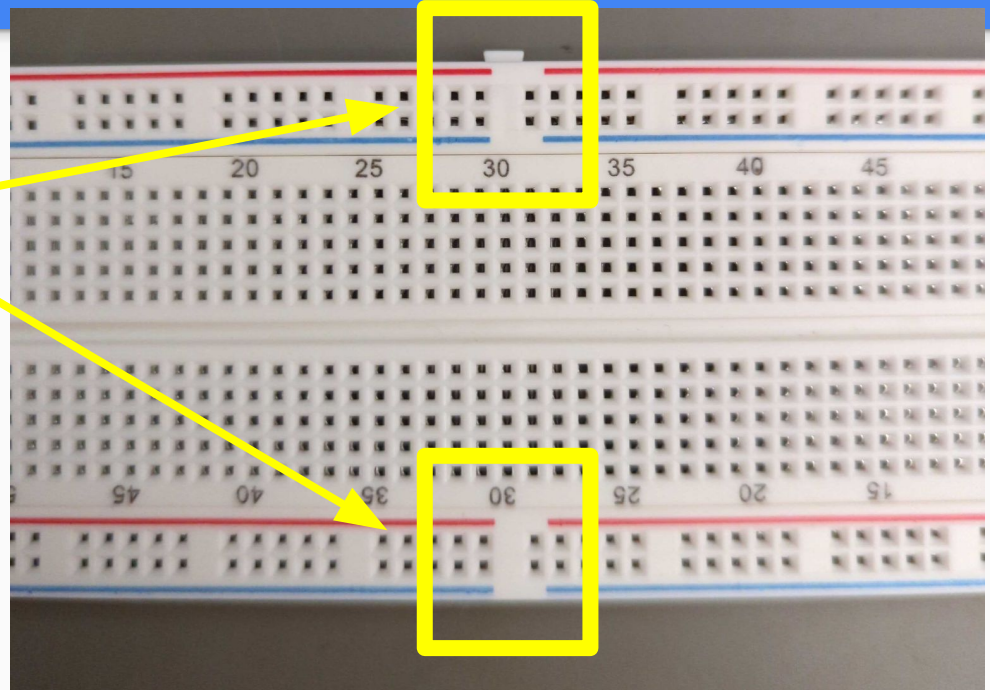
# Caution!

- Some breadboards may have a break in the power and ground rails
- Make sure to connect them with wires (4 total)!




# Motor Controller Circuits

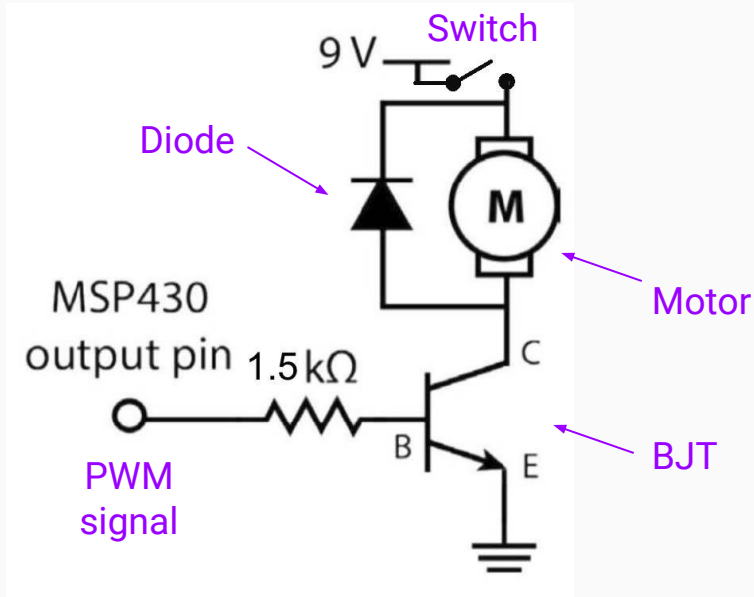

- We'll be building this circuit twice
  - Many new components!
- In the motor unit tests, we'll run over a range of **PWM values** to see the motors speed up and slow down


# Pulse Width Modulation (PWM)

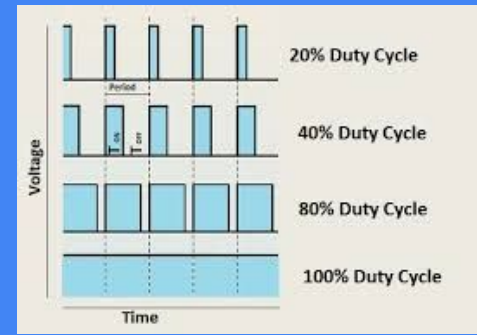


- Square wave with variable “on” time
  - “Duty cycle” is the percentage of time the signal spends “on” or at its “high” in one period
  - If period  $T = 1\text{ s}$ , then 50% duty cycle means it spends .5s “on” and .5s “off”
- Method of supplying variable amounts of power to a component
  - We will be using this to control our motors
- Motors and multimeters unable to “react fast enough” to the rapid turning on and off, so see averaged-out analog voltage depending on duty cycle
  - Variable frequency, anywhere from a few hundreds to thousands of Hz
  - If “on” voltage is 3.3V, then 50% duty cycle means you see 1.65V
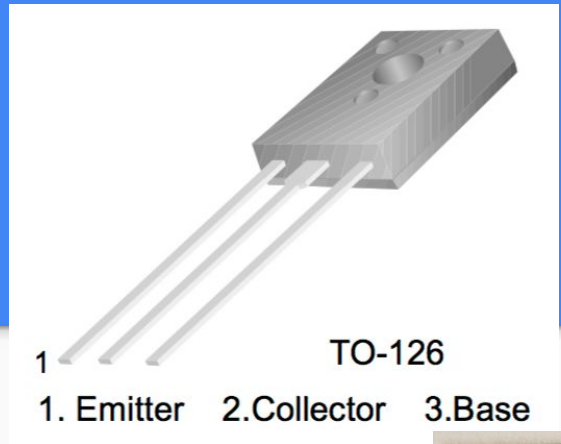
# New Component: BJT


- Bipolar Junction Transistor
  - 3 pins: Base (B), Collector (C), Emitter (E)
  - Analogous to MOSFETs: Base -> Gate, Collector -> Drain, Emitter -> Source
- NPN BJT behaves similarly to NMOS
  - High Base voltage turns BJT “on” and conducts current from Collector to Emitter
  - High Gate voltage turns NMOS “on” and conducts current from Drain to Source
  - More accurate model description in lab note
- NOT the voltage regulator component
  - Body is fully black plastic, does not have a metal tab sticking up
  - Orientation of the picture is with the 3 dots on the plastic body facing you



# NPN BJT Model

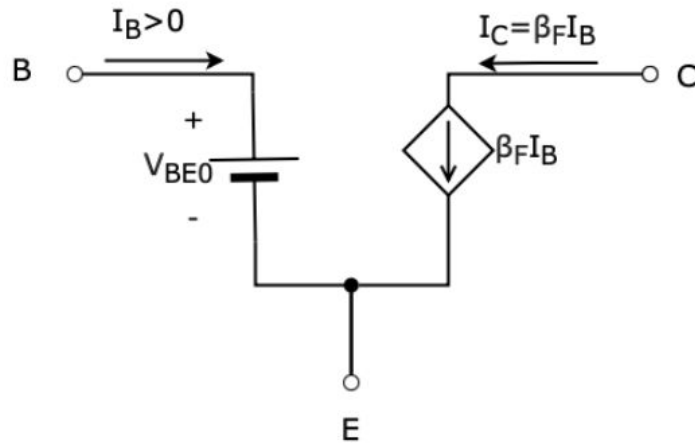

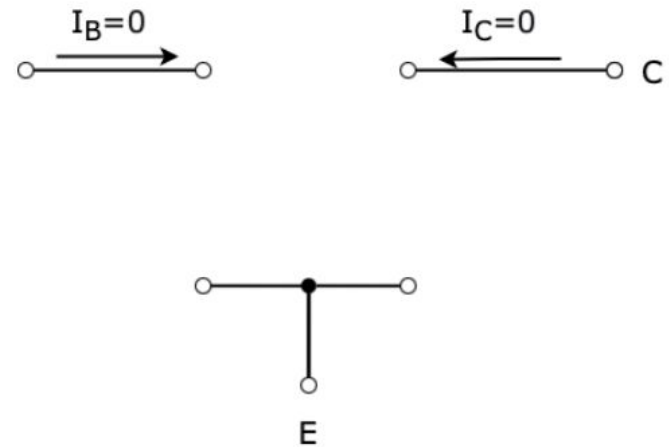(a) Model of BJT in ON mode (when MSP430 output pin is HIGH)



(b) Model of BJT in OFF mode (when MSP430 output pin is LOW)

Figure 3: Model of NPN BJT in Different Modes




# New Component: Switch




- Middle pin is ALWAYS shorted (connected) to something
  - If switch is in the left position, left and middle pins are shorted together
  - If switch is in right position, right and middle pins are shorted together
- Connect your motors to middle pin, 9V to side pin, GND to other side pin
  - Toggle your motors being connected to 9V and GND
- **DO NOT CONNECT 9V OR GND TO MIDDLE PIN**
  - You will short 9V to GND if you flip the switch
  - Fastest way to say goodbye to your circuit, battery, and breadboard
  - **DON'T DO IT!**
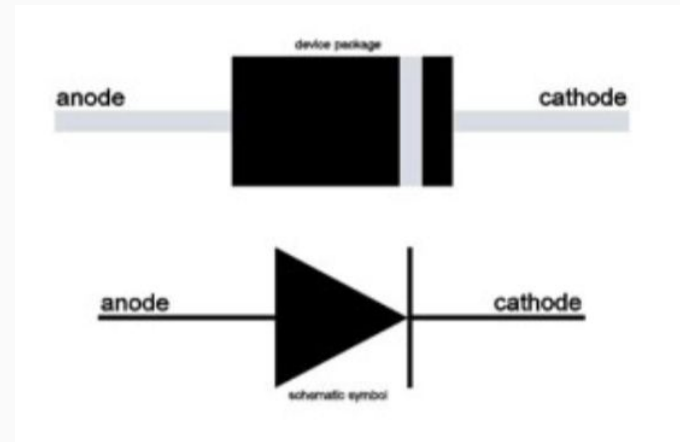
# New Component: Diode


- Anode is +
- Cathode is -
- **Direction is important**
  - Diodes conduct current one way but not the other
  - Make sure you double check that you have connected it in correct direction
- **not light emitting!**


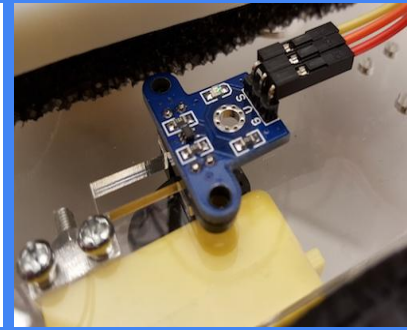
# New Component: Encoders (Photointerrupters)



- Beam of light between 2 “legs”
- As wheel turns, rotates encoder wheel with it
  - Encoder wheel has many holes in it
  - As wheel rotates, spokes block and holes unblock the beam of light
- Can calculate velocity of car from rate of encoder value change
- 3 pins
  - “G” = ground, connect to breadboard 0V negative rail
  - “V” = voltage, connect to breadboard 3.3V positive rail from output of 3.3V regulator, NOT Arduino’s 3.3V pin
  - “S” = encoder signal; input to voltage divider whose output goes to Arduino pins (2 and 3)

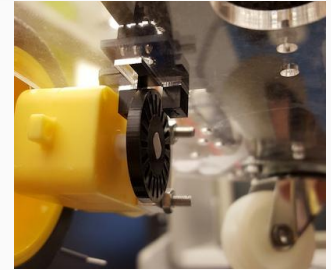


# Testing Encoders

- Encoder “S” pins connected to voltage divider
  - Using resistors of  $\geq 1k$ , divide the 3.3V max voltage down to between 2V - 2.5V
  - Can accomplish with one 1k ohm and one 2k ohm resistor
- Pass something between encoder legs or turn car wheel, red LED on encoder should blink if powered correctly
- `encoder_test_0_ticks.ino`
  - 4 phases: both wheels unpowered, L wheel powered, R wheel powered, both wheels powered
  - Test once with encoder wheels OFF
    - Checks if encoder readings are from noise or from actual car movement
  - Then test with encoder wheels ON
    - Rules out false negative

# Arduino Stuff

- Make sure to connect one of your GND pins (any one works) to your breadboard negative (-) rail (which carries GND)
- DO NOT connect the 3V3 or 5V pin to anything for this lab!
- Pins can only tolerate voltages between 0V and 5V.

# BREADBOARD LAYOUT

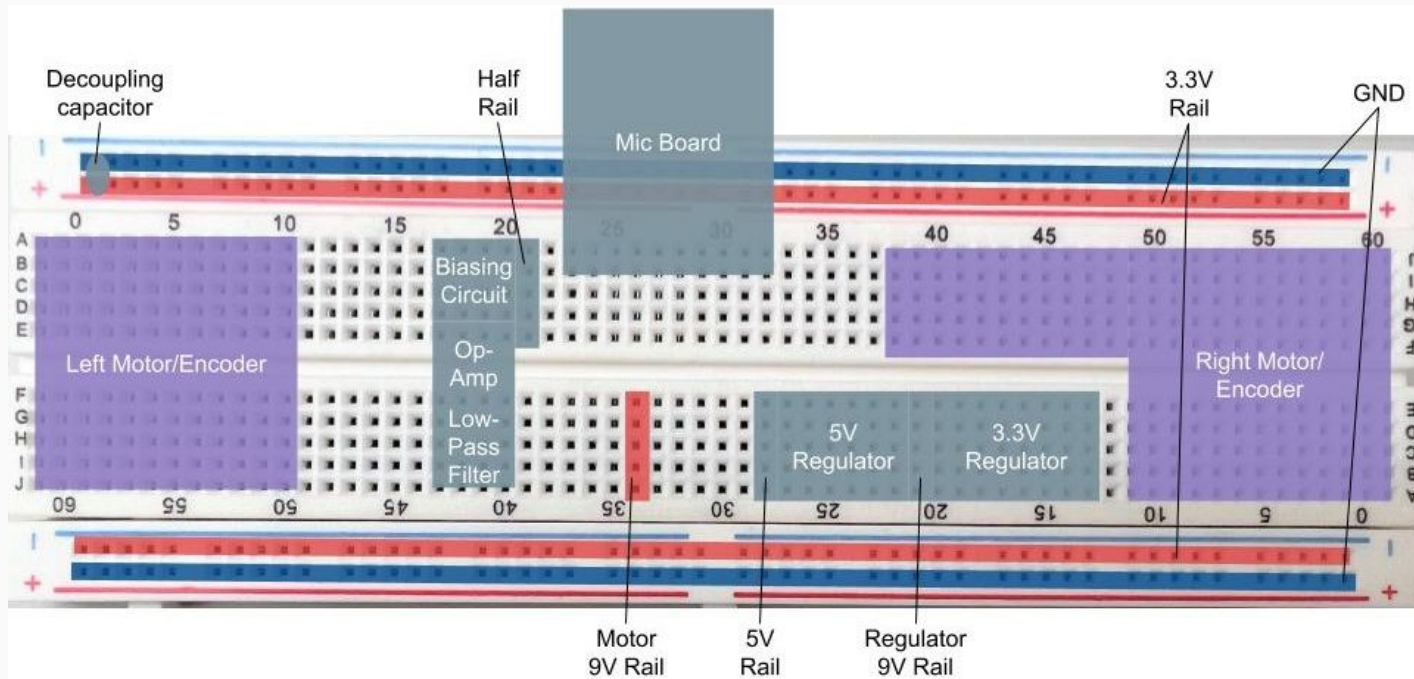

# Lab 3 Checkoff

- **Follow ALL instructions clearly in ipynb!**
- Requirements for checkoff:
  - Have read lab note
  - Demonstrate both motors responding to changes in duty cycle
  - Demonstrate encoder tests passing
  - Desk should be cleaned.
  - **Be prepared to answer conceptual checkoff questions!**

**Checkoff and help queues close 10 minutes before the end of section.**

Let's get into it!



# Important Forms/Links

- Help request form: <https://eecs16b.org/lab-help>
- Checkoff request form: <https://eecs16b.org/lab-checkoff>
- Extension Requests: <https://eecs16b.org/extensions>
- Makeup Lab: <https://makeup.eecs16b.org>
- Slides: <links.eecs16b.org/lab3-slides>
- Anon Feedback: <https://eecs16b.org/lab-anon-feedback>
- Lab Groups: <https://eecs16b.org/lab-groups>